

Lab Report – Experiment 1: Ramp Generator

Objective

To design, simulate, and experimentally verify a ramp (triangle) wave generator using:

- An **LM324 op-amp** integrator
 - An **LM339 comparator** with hysteresis
 - A feedback loop that sustains oscillation.
-

Theory

A ramp generator produces a periodic triangular waveform by integrating a square wave. In this design:

1. **LM339 comparator:**

- Configured as a **Schmitt trigger**.
- Switches output polarity when the ramp crosses defined thresholds.
- Feedback resistors (R2, R3) set the hysteresis width.


2. **LM324 op-amp integrator:**

- Converts comparator's square wave into a ramp (triangle wave).
- Integrates constant high/low levels, producing a rising or falling voltage.

3. **Positive Feedback Loop:**

- Comparator output → Integrator → Comparator input.
 - Oscillation frequency depends on **R1, C1, hysteresis**.
-

Circuit Parameters Used

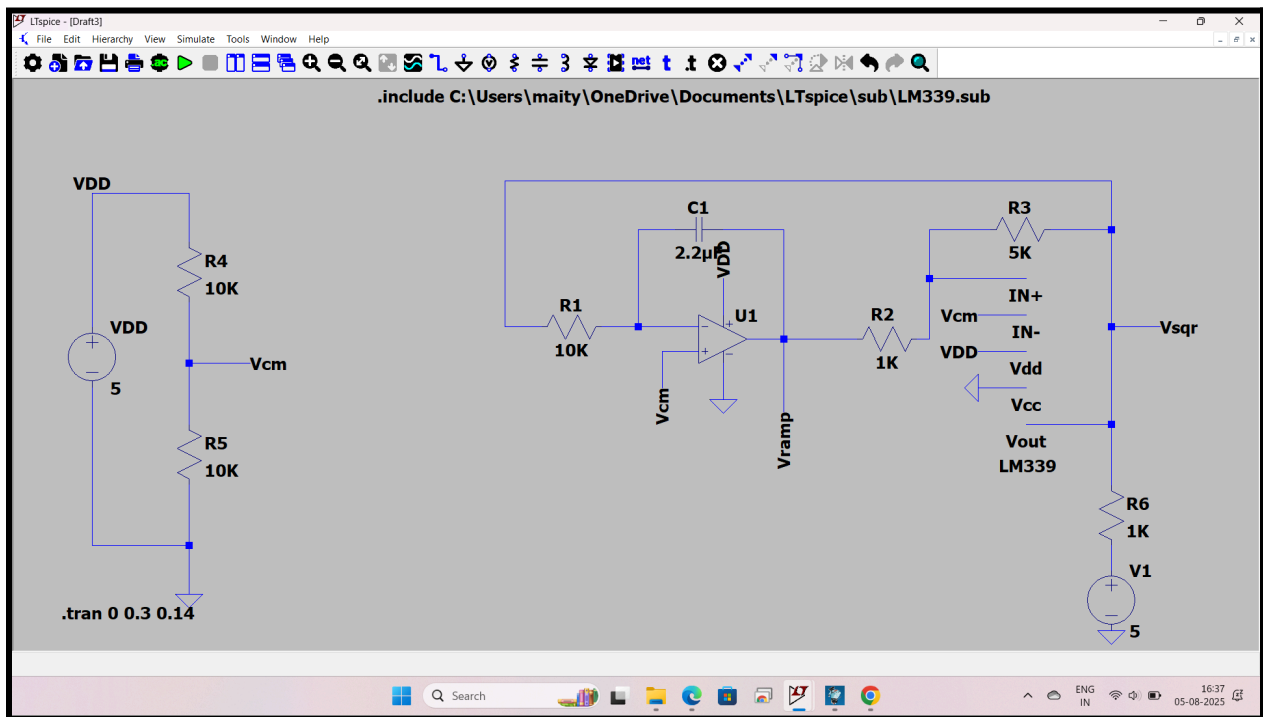

Component	Value	Purpose
R1	10 kΩ	Integrator input resistor
R2	1 kΩ	Hysteresis network
R3	5 kΩ	Hysteresis network
C1	2.2 μF	Integrator capacitor
Pull-up resistor	1 kΩ	LM339 output pull-up
Op-amp	LM324	Integrator
Comparator	LM339	Schmitt trigger
VDD	5 V	Power supply

Simulation Results (LTspice)

- **Vramp**: Triangular waveform, peak-to-peak $\approx 0.8\text{ V}$ – 0.9 V , centered around $\sim 2.5\text{ V}$.
- **Vsqr**: Square wave, amplitude ≈ 0 – 5 V .

- Oscillation period $\approx 40 \text{ ms}$ \rightarrow frequency $\approx 25 \text{ Hz}$.


Experimental Results (ADALM1000)

Signal	Waveform Shape	Peak-to-Peak	Average DC
Vramp (Integrator Output)	Triangle	$\sim 2.13 \text{ V}$	$\sim 2.55 \text{ V}$
Vsqr (Comparator Output)	Square	$\sim 4.31 \text{ V}$	$\sim 2.41 \text{ V}$

The hardware output matches simulation in **waveform shape** but differs in **amplitude and frequency** due to:

- Larger capacitor ($2.2 \mu\text{F}$ \rightarrow much slower ramp).
- Low pull-up resistor ($1 \text{ k}\Omega$ \rightarrow higher load, affecting switching speed).
- Component tolerances.


Waveforms

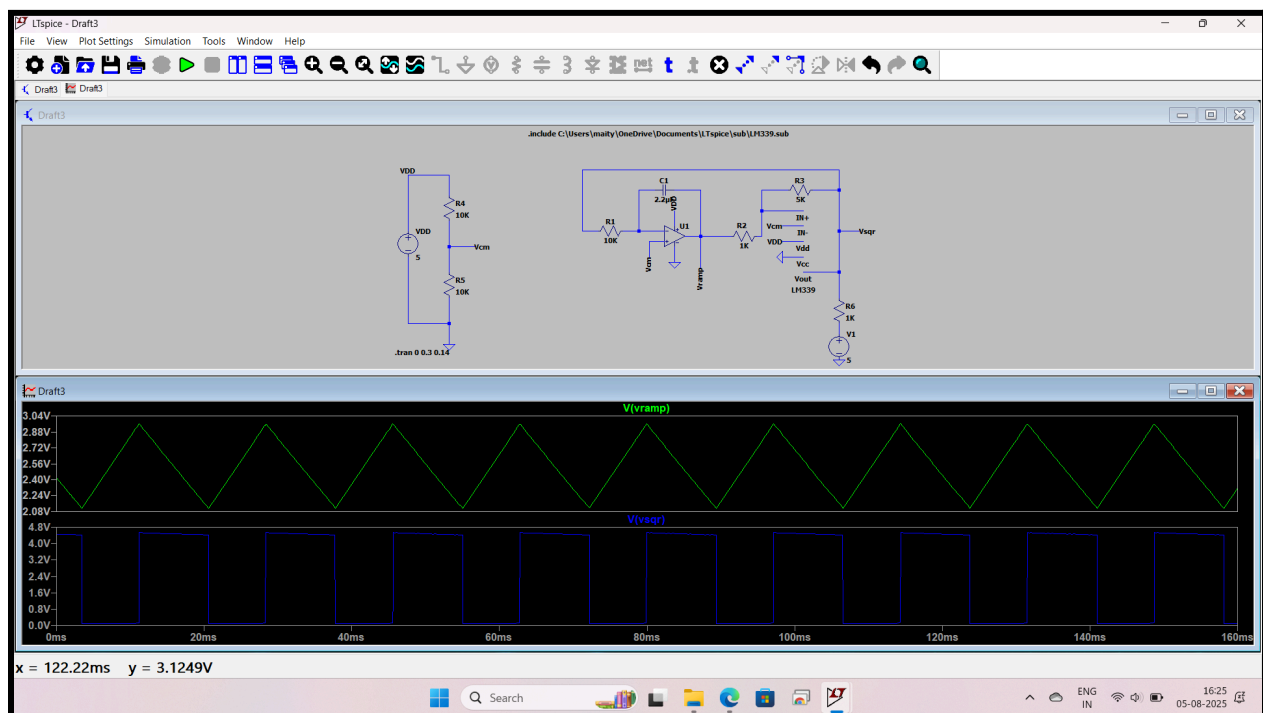

Simulation – LTspice

- Vramp: Green triangular wave.
- Vsqr: Blue square wave.

Experimental – ADALM1000 (Pixelpulse2)

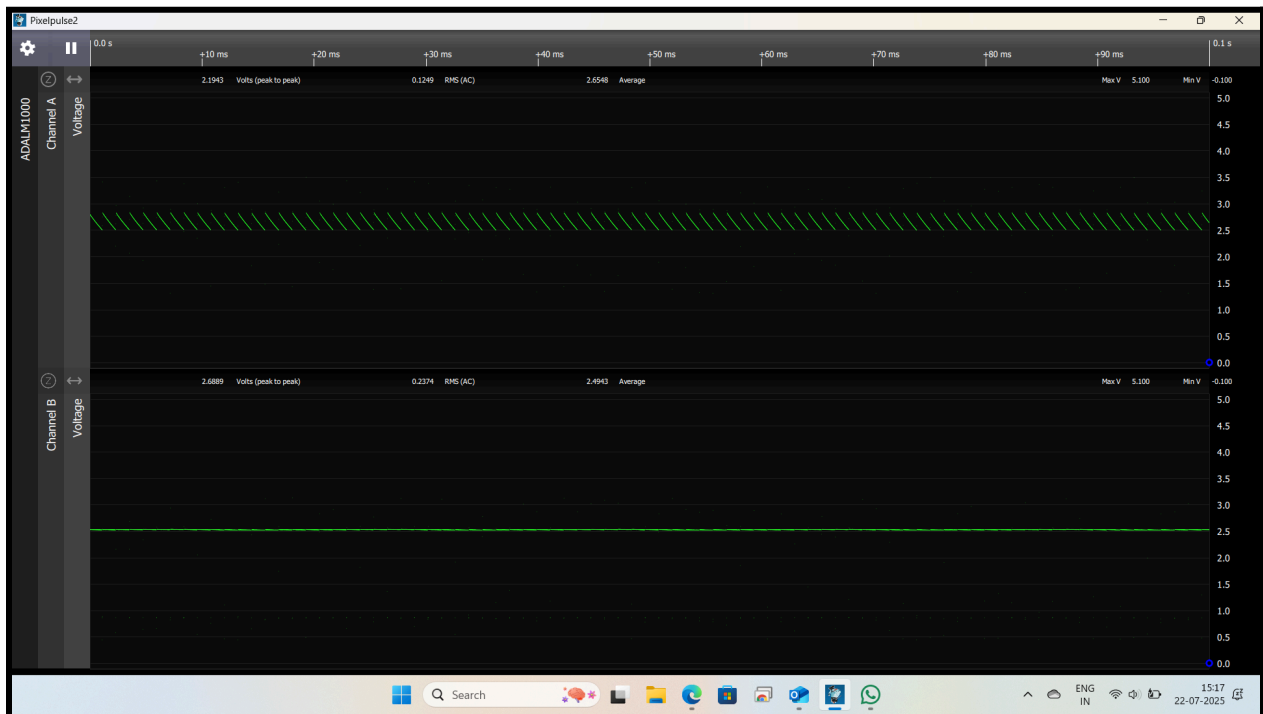

- Channel A (Vramp): Triangular wave, ~2.13 Vpp.
- Channel B (Vsqr): Square wave, ~4.31 Vpp.

Observations

1. Increasing $C1 \rightarrow$ lowers oscillation frequency (slower ramp).
2. Low-value pull-up resistor ($1\text{ k}\Omega$) \rightarrow increases current draw and may distort output.
3. Hysteresis network ($R2/R3$) determines amplitude of Vramp.
4. The integrator output average remains close to $V_{CM} \approx 2.5\text{ V}$.

Conclusion

The ramp generator using LM324 + LM339 works as expected:

- Simulation and hardware results both show proper triangular and square waveforms.
- Differences in frequency/amplitude are due to selected component values (especially C1).
- This confirms the theory that an integrator + Schmitt trigger can sustain oscillations and produce ramp signals.